


Nirma University
Institute of Technology
School of Engineering
Electrical Engineering Programme
2EE304: Analog and Digital Electronic Circuits

Assignment – 1


Issue Date: 13th September 2019

Submission Date: 19th September 2019

 
- Q.1 For the network shown below:
- Determine Z_i and Z_o .
 - Calculate A_v and A_i .
 - Determine r_e and compare βr_e to h_{ie} .



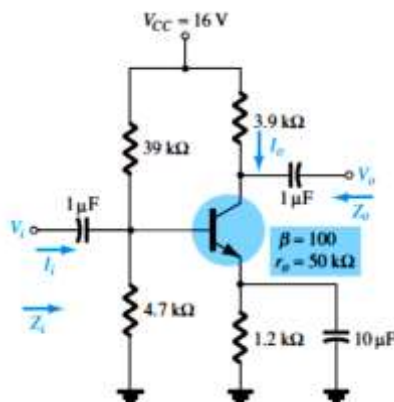- Q.2 For the network shown below :
- Determine r_e .
 - Calculate Z_i and Z_o .
 - Find A_v .



 - Q.3 Explain the analysis of common emitter, emitter biasing circuit with and without bypass capacitor in r_e model and also derive voltage gain, current gain, input resistance and output resistance.
- Q.4 Discuss the evolution of differential amplifier.
- Q.5 For the given cascaded amplifier shown in figure, calculate Q-point of both transistors, input impedance, output impedance, overall gain and values of bypass capacitors. Take $V_{BE}=0.6\text{ V}$ and $\beta=99$.



- Q.6 What is a level translator circuit? Why is it used with the cascaded differential amplifier?
- Q.7 Prove that conventional amplifier follows exponential transfer characteristics whereas differential amplifier follows tanh transfer characteristics.
- Q.8 Boolean function has minterms as 2,4,5,7,12,13,15,17,23,27,30 design the circuit by using K-map. Take 11 and 18 as don't cares.
- Q.9 Prove that NAND and NOR gates are universal gates.
- Q.10 Prove that SOP and POS forms of Boolean equations are inverse of each other by taking suitable example.
- Q.11 Implement the full adder circuit and full subtractor circuit with NOR logic only.
- Q.12 Design 16x1 multiplexer using two 8x1 multiplexers.
- Q.13 Convert Active high SR latch into Active low SR Latch
- Q.14 Discuss the applications of Multiplexers and De-Multiplexers
- Q.15 Design a Logic Circuit of BCD to seven Segment display
